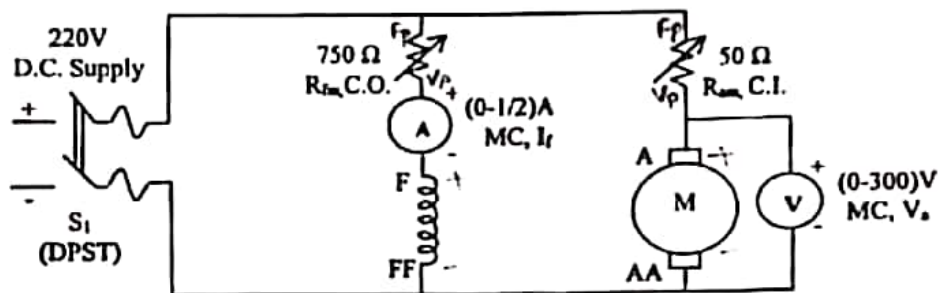


## Experiment no.: 2 Speed control of D.C. shunt motor

**Aim:** To control the speed of the given D.C shunt motor by a) Armature control and b) Field control and to plot the speed variations.

<b>Apparatus Required:</b> D.C. Shunt Motor	- 01
Ammeter (0 - 1/2)A, MC	- 01
Voltmeter (0 - 300)V, MC	- 01
Rheostat (50 Ω)	- 01
Rheostat (750 Ω)	- 01
Tachometer	- 01
Patch cords	- 02
Connecting wires	- 01

**Circuit Diagram:**



Name plate details D.C. Shunt Motor	
P =	I <sub>f</sub> =
V =	N =
I <sub>L</sub> =	

**Procedure:**

1. Connections are made as shown in the circuit diagram.
  2. Keeping the rheostats R<sub>am</sub> in cut-in and R<sub>fm</sub> in cut-out, the supply switch S<sub>1</sub> is closed.
- a). Armature Control:**
3. By operating R<sub>fm</sub>, the field current I<sub>f</sub> is adjusted to a particular value ( I<sub>n</sub> ). The readings of ammeter, voltmeter and speed of the motor are noted down.
  4. The armature voltage V<sub>a</sub> is varied in steps by operating R<sub>am</sub>. At each step the reading of the voltmeter and speed are noted down. (At each step the field current I<sub>f</sub> must be constant).
  5. Brought R<sub>am</sub> to cut-in position, the steps 3 and 4 are repeated for another particular value of field current I<sub>n</sub>.
  6. Finally R<sub>fm</sub> and R<sub>am</sub> rheostats are brought to their original positions and the supply switch S<sub>1</sub> is opened.
- b). Field Control:**
3. By operating R<sub>am</sub>, the armature voltage V<sub>a</sub> is adjusted to a particular value ( V<sub>a1</sub> ). The readings of voltmeter, ammeter and the speed of the motor are noted down.
  4. The field current I<sub>f</sub> is varied in steps by operating R<sub>fm</sub>. At each step the reading of the ammeter and the speed are noted down. (At each step the armature voltage V<sub>a</sub> must be constant).
  5. Brought R<sub>fm</sub> to cut-out position, the steps 3 and 4 are repeated for another particular value of armature voltage V<sub>a2</sub>.
  6. Finally, R<sub>fm</sub> and R<sub>am</sub> rheostats are brought to their original positions and the supply switch S<sub>1</sub> is opened.

**Tabular Column:**


**a). Armature Control:**

Sl.No.	$I_{\Omega} =$ Amps		$I_{\Omega} =$ Amps	
	$V_a$ Volts	N rpm	$V_a$ Volts	N rpm


**b). Field Control:**

Sl.No.	$V_{a1} =$ Volts		$V_{a2} =$ Volts	
	$I_f$ Amps	N rpm	$I_f$ Amps	N rpm

**Graphs:**

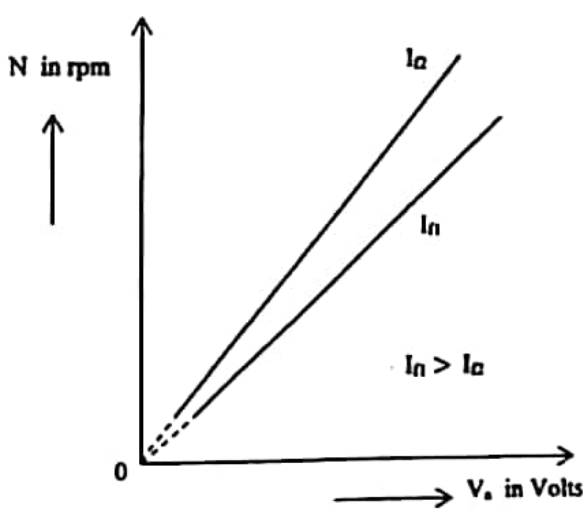

a). Armature Control

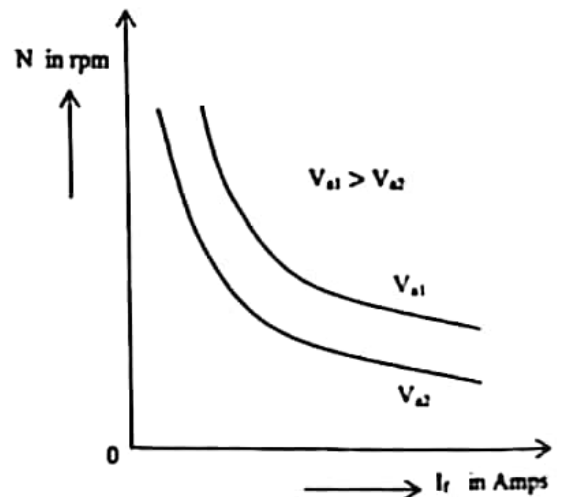

b). Field Control


## Experiment no.: 1 Load test on D.C. shunt motor

**Aim:** To conduct load test on a D.C shunt motor and to plot its performance characteristics

**Apparatus Required:**

D.C. Motor- D.C. Generator set	- 01
Ammeter (0 – 10/20)A, MC	- 02
Voltmeter (0 - 300)V, MC	- 02
Rheostat (19Ω)	- 01
Rheostats (750 Ω)	- 02
Loading rheostat	- 01
Tachometer	- 01
Patch cords	- 04
Connecting wires	- 13

**Circuit Diagram:**

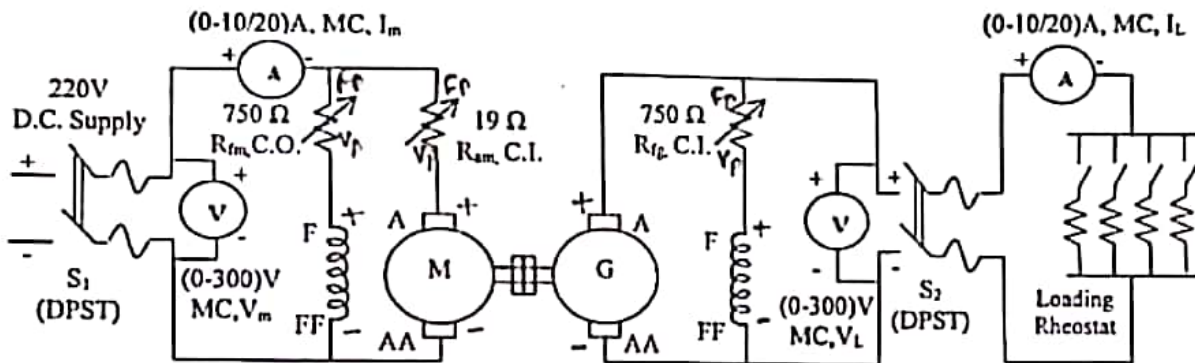

Name plate details	
D.C. Motor	D.C. Generator
P =	P =
V =	V =
IL =	IL =
I <sub>r</sub> =	I <sub>r</sub> =
N =	N =

**Procedure:**

1. Connections are made as shown in the circuit diagram.
2. Keeping the rheostats  $R_{am}$  in cut-in,  $R_{fm}$  in cut-out,  $R_{fg}$  in cut-in and load switch  $S_2$  open, the supply switch  $S_1$  is closed.
3. The motor is brought to its rated speed (1500 rpm) by first cutting-out  $R_{am}$  completely and then slowly cutting-in the  $R_{fm}$ , if necessary.
4. The generator voltage  $V_L$  is build up to the rated value of 220V by cutting-out  $R_{fg}$  gradually. Then the no-load readings of all the meters are noted down.
5. The load switch  $S_2$  is closed. Using loading rheostat the load is increased in steps. At each step, the generator voltage ( $V_L$ ) is kept constant at rated value by gradually cutting-out the  $R_{fg}$  and the readings of all the meters and speed (using Tachometer) are noted down.
6. The loading of the motor is continued till the current drawn by the motor equals to its rated value.
7. The load is decreased and at the same time maintain  $V_L$  constant by cutting-in the  $R_{fg}$  and the load switch  $S_2$  is opened.
8. Now, brought  $R_{fg}$  to cut-in position, and then  $R_{fm}$  and  $R_{am}$  to cut-out and cut-in positions respectively. Finally, open the supply switch  $S_1$ .

**Tabular Column:**

Sl.No.	N rpm	I <sub>m</sub> Amps	V <sub>m</sub> Volts	I <sub>l</sub> Amps	V <sub>l</sub> Volts	% η	B.H.P (HP)	T N-m

**Calculations:**

$P_{in}$  = Power input to the motor =  $V_m \times I_m = \underline{\hspace{2cm}}$  Watts

$P_{out}$  = Power output of the motor = Power input to the generator

$\therefore P_{out} = \frac{\text{Power output of the generator}}{\text{Efficiency of the generator}} = \frac{V_L \times I_L}{\eta_g} = \underline{\hspace{2cm}}$  Watts



Assume, efficiency of the generator  $\eta_g = 0.75$  (i.e, 75%)

Percentage efficiency (% η) of the motor =  $\frac{P_{out}}{P_{in}} \times 100 = \underline{\hspace{2cm}}\%$

B.H.P =  $\frac{P_{out}}{735.5} = \underline{\hspace{2cm}}$  H.P

Torque (T) =  $\frac{P_{out} \times 60}{2\pi \times N} = \underline{\hspace{2cm}}$  N-m

**Graphs:**

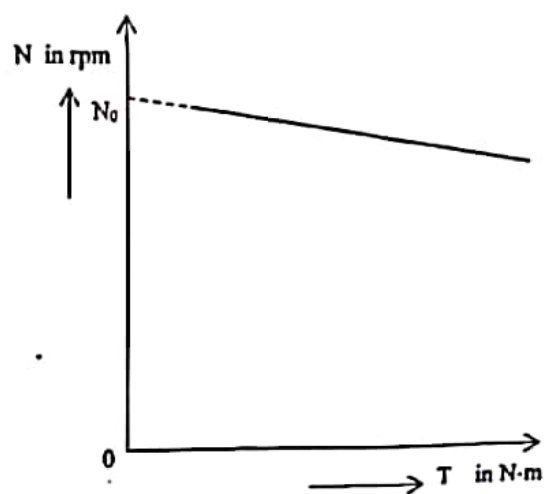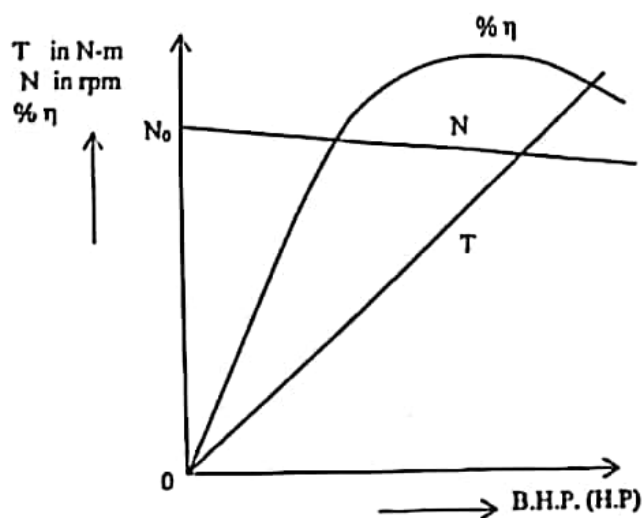


### Experiment no.: 9 3 Swinburne's Test

**Aim:** To conduct Swinburne's test or no-load test on a given D.C shunt machine to obtain its efficiency.

**Apparatus Required:**

D.C. Shunt machine	- 01
Ammeter (0 – 5/10)A, MC	- 01
Ammeter (0 – 1/2)A, MC	- 01
Voltmeter (0 - 300)V, MC	- 01
Rheostat (19Ω)	- 01
Rheostats (750 Ω)	- 01
Tachometer	- 01
Patch cords	- 02
Connecting wires	- 08

**Circuit Diagram:**

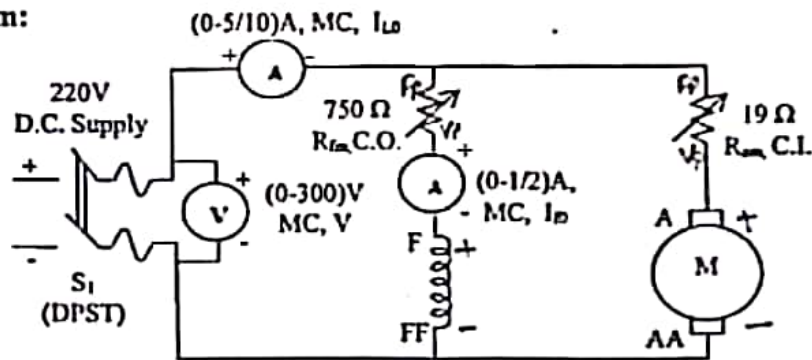

Name plate details D.C. Shunt Motor	
P =	Ir =
V =	N ≅
IL =	

**Procedure:**

1. Connections are made as shown in the circuit diagram.
2. Keeping the rheostats  $R_{sm}$  in cut-in and  $R_{fm}$  in cut-out, the supply switch  $S_1$  is closed.
3. The motor is brought to its rated speed (1500 rpm) by first cutting-out  $R_{sm}$  completely and then slowly cutting-in the  $R_{fm}$ , if necessary.
4. The readings of ammeters and voltmeter are noted down.
5. Finally,  $R_{fm}$  and  $R_{sm}$  rheostats are brought to their original positions and the supply switch  $S_1$  is opened.
6. Armature resistance of the machine ( $R_a$ ) is measured across the terminals A-AA using multimeter.

**Tabular Column:**

Sl.No.	V Volts	$I_{L0}$ Amps	$I_{f0}$ Amps	$R_a$ Ohms
1				

**Calculations:** At no-load:

Power input to the motor =  $V \times I_{L0} =$  \_\_\_\_\_ Watts

Armature copper loss =  $(I_{L0} - I_{f0})^2 \times R_a =$  \_\_\_\_\_ Watts

Constant losses,  $W_c = (\text{Power input}) - (\text{Armature copper loss}) =$  \_\_\_\_\_ Watts

a) Efficiency of the machine when running as motor: At full load:

Note down full load current or rated current  $I_L$ , rated field current  $I_f$  of the motor from the name plate details.

Armature current of the motor,  $I_a = (I_L - I_f) = \underline{\hspace{2cm}}$  Amps

Armature copper loss =  $I_a^2 \times R_a = \underline{\hspace{2cm}}$  Watts

Power input to the motor =  $P_{in} = V \times I_L = \underline{\hspace{2cm}}$  Watts

Total losses =  $W_c + \text{Armature copper loss} = \underline{\hspace{2cm}}$  Watts

Power output of the motor =  $P_{out} = (\text{Power input}) - (\text{Total losses}) = \underline{\hspace{2cm}}$  Watts

Percentage efficiency ( $\% \eta_m$ ) of the motor at full load =  $\frac{P_{out}}{P_{in}} \times 100 = \underline{\hspace{2cm}}\%$

Similarly efficiencies at 75%, 50% & 25% of full load are determined and results are tabulated.

b) Efficiency of the machine when running as generator: At full load:

Note down full load current or rated current  $I_L$ , rated field current  $I_f$  of the generator from the name plate details.

Armature current of the generator,  $I_a = (I_L + I_f) = \underline{\hspace{2cm}}$  Amps

Armature copper loss =  $I_a^2 \times R_a = \underline{\hspace{2cm}}$  Watts

Power output to the generator =  $P_{out} = V \times I_L = \underline{\hspace{2cm}}$  Watts

Total losses =  $W_c + \text{Armature copper loss} = \underline{\hspace{2cm}}$  Watts


Power input of the generator =  $P_{in} = (\text{Power output}) + (\text{Total losses}) = \underline{\hspace{2cm}}$  Watts

Percentage efficiency ( $\% \eta_g$ ) of the generator at full load =  $\frac{P_{out}}{P_{in}} \times 100 = \underline{\hspace{2cm}}\%$

Similarly efficiencies at 75%, 50% & 25% of full load are determined and results are tabulated.

Sl.No.	Load current $I_L$ Amps	$\% \eta_m$	$\% \eta_g$
1	Full load		
2	75% full load		
3	50% full load		
4	25% full load		

Graph:

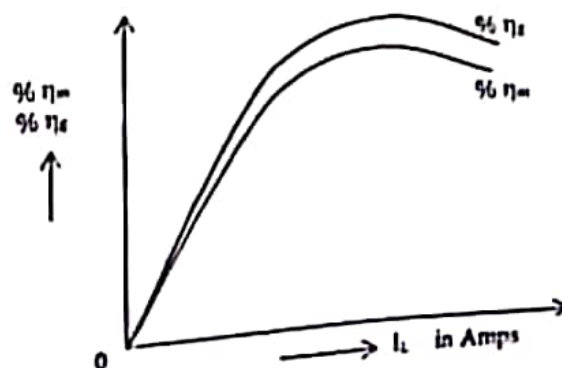

Experiment no.: 4


**Load Test on Single Phase Induction Motor**

**Aim:** To conduct load test on the given single phase induction motor and to determine its percentage efficiency, BHP, torque, slip and draw the performance characteristics.

**Apparatus Required:**

1 $\phi$ Induction Motor - D.C. Generator set	- 01
1 $\phi$ Auto Transformer	- 01
Ammeter (0 - 5/10)A, MI	- 01
Voltmeter (0 - 300)V, MI	- 01
Wattmeter (0 - 5/10)A, 250V, UPF	- 01
Ammeter (0 - 2.5/5)A, MC	- 01
Voltmeter (0 - 300)V, MC	- 01
Rheostat (1200 $\Omega$ )	- 01
Lamp load	- 01
Tachometer	- 01
Patch cords	- 06
Connecting wires	- 12

**Circuit Diagram:**

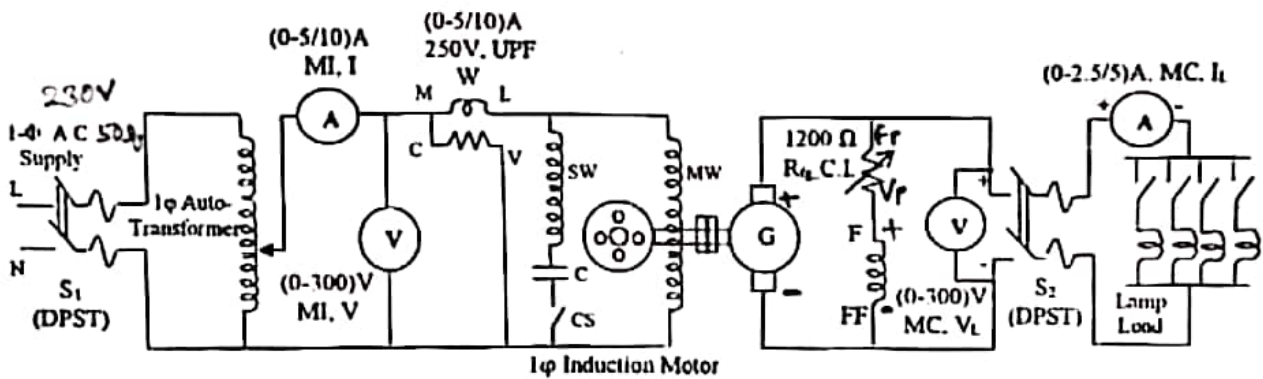

SW- Start Winding. MW - Main Winding. C - Capacitor. CS - Centrifugal Switch

L - Line / phase

N - Neutral

Name plate details	
1 $\phi$ Induction Motor	D.C. Generator
Power =	f =
V =	Power =
I =	V =
N =	$I_L$ =
P = Poles =	$I_f$ =
	N =

**Procedure:**

1. Connections are made as shown in the circuit diagram.
2. Keeping the load switch  $S_2$  open and  $R_{fg}$  in cut-in position, the supply switch  $S_1$  is closed.
3. Using 1 $\phi$  auto-transformer the supply voltage is gradually increased to rated value (230V).
4. Now, the d.c. generator voltage is build up to its rated value of 220V by cutting out of  $R_{fg}$ .
5. Corresponding to this no load, the readings of all the meters & the speed are noted.
6. The induction motor is indirectly loaded by loading the d.c. generator, i.e., close the load switch  $S_2$  & with the help of lamp load, the d.c. generator is loaded in steps until the ammeters I reads the rated current of the induction motor. At each step, the d.c. generator terminal voltage is maintained constant at its rated value (220V) using  $R_{fg}$  and the readings of all the meters and speed are noted.

K-11

7. The load is decreased in steps, maintaining the terminal voltage of the d.c. generator constant using  $R_{tf}$  and the load switch  $S_2$  is opened.
8. Now,  $R_{tf}$  is brought to cut in position then, 1 $\phi$  auto-transformer to zero output position & the supply switch  $S_1$  is opened.

**Tabular Column:**

Sl. No.	V Volts	I Amps	$W = W_R \times K$ Watts	$V_L$ Volts	$I_L$ Amps	N rpm	% $\eta$	B.H.P (HP)	T N-m	% slip	p.f.
1											
2											
3											
4											
5											

$W_R$  = Wattmeter Reading,

$$K = \text{Wattmeter constant} = \left[ \frac{(\text{Voltage range}) \times (\text{Current range}) \times (\text{p.f. of wattmeter})}{\text{Full scale divisions of wattmeter}} \right]$$

**Calculations: From Load Readings:**

$$P_{og} = \text{Power output of the d.c. generator} = V_L \times I_L = \text{_____ Watts}$$

Assume efficiency of d.c. generator = 0.8

$$P_{out} = \text{Power output of induction motor} = \text{Power input to d.c. generator} = \frac{P_{og}}{0.8} = \text{_____ Watts}$$

$$P_{in} = \text{Power input to the induction motor} = W = \text{_____ Watts}$$

$$\text{Percentage efficiency of the Induction motor} = \% \eta = \frac{P_{out}}{P_{in}} \times 100 = \text{_____ \%}$$

$$\text{B.H.P} = \frac{P_{out}}{735.5} = \text{_____ H.P.}$$

$$\text{Torque (T)} = \frac{P_{out} \times 60}{2\pi \times N} = \text{_____ N-m}$$



$$N_s = \text{Synchronous speed of induction motor} = \frac{120 \times f}{p} = \text{_____ rpm}$$



$$\% s = \text{Percentage slip of induction motor} = \frac{N_s - N}{N_s} \times 100 = \text{---}\%$$

$$\text{p.f} = \text{Power factor} = \cos\phi = \frac{W}{V \times I}$$

**Graphs:**

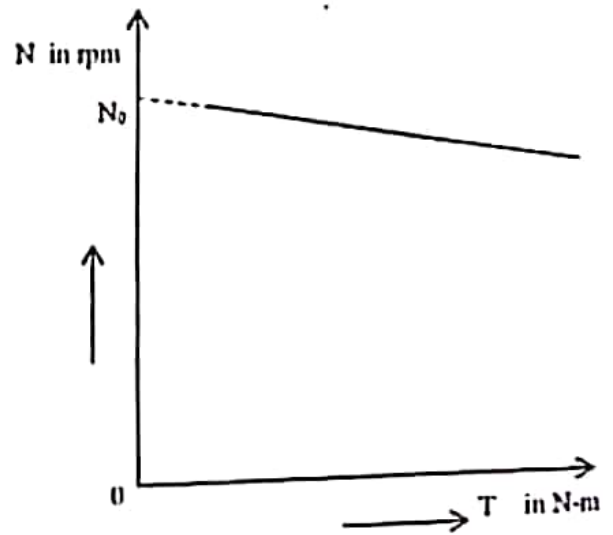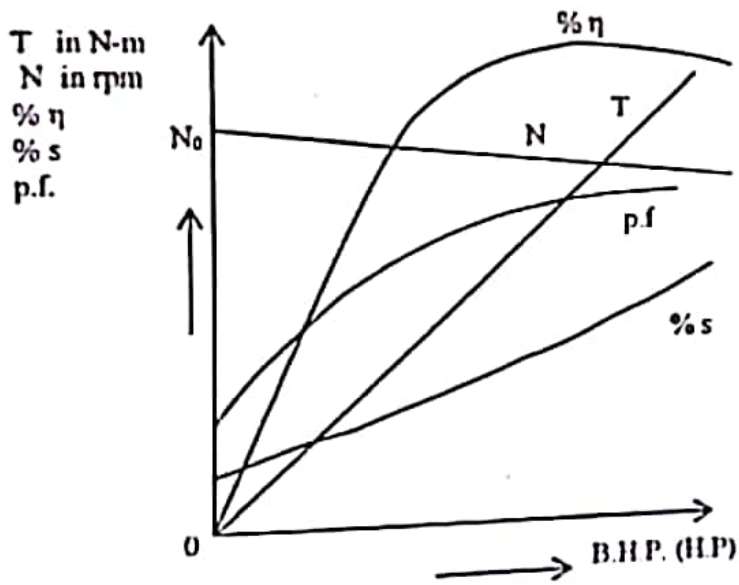


## Experiment no.: 5 Load Test on Three Phase Induction Motor

**Aim:** To conduct load test on the given three phase induction motor and to determine its percentage efficiency, BHP, torque, slip and draw the performance characteristics.

**Apparatus Required:**

3 $\phi$ Induction Motor - D.C. Generator set	- 01
Ammeter (0 - 5/10)A, MI	- 02
Voltmeter (0 - 600)V, MI	- 01
Wattmeter (0 - 5/10)A, 500V, UZF	- 02
Ammeter (0 - 10/20)A, MC	- 01
Ammeter (0 - 1/2)A, MC	- 01
Voltmeter (0 - 300)V, MC	- 01
Rheostat (750 $\Omega$ )	- 01
Loading rheostat	- 01
Tachometer	- 01
Patch cords	- 08
Connecting wires	- 20

**Circuit Diagram:**

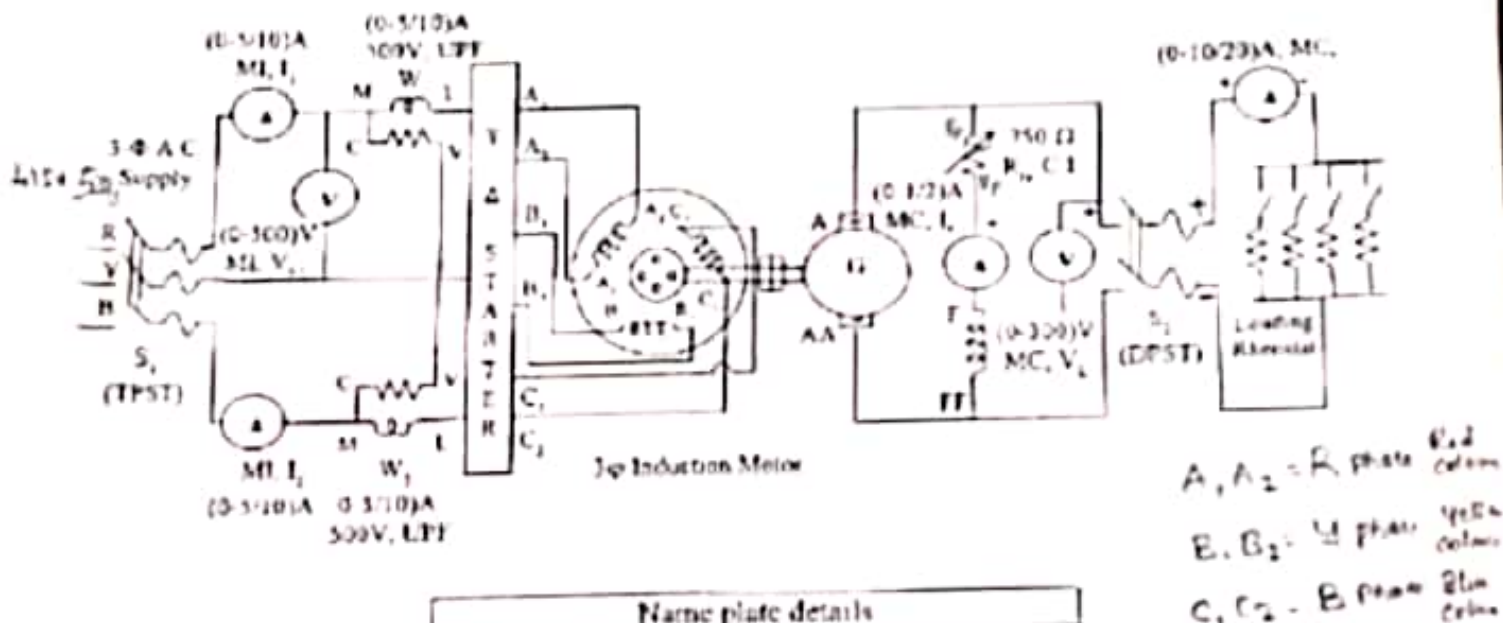

Name plate details	
3 $\phi$ Induction Motor	D.C. Generator
Power =	Power =
$V_1$ =	V =
$I_L$ =	$I_L$ =
N =	$I_r$ =
P = Poles =	N =

**Procedure:**

1. Connections are made as shown in the circuit diagram
2. Keeping the load switch  $S_2$  open and  $R_g$  in cut-in position, the supply switch  $S_1$  is closed.
3. The induction motor is started using the star-delta (Y- $\Delta$ ) starter.
4. Now, the d.c. generator voltage is build up to its rated value of 220V by cutting out of  $R_g$
5. Corresponding to this no load, the readings of all the meters & the speed are noted. If any of the wattmeters 'kick back', then its potential coil terminals common (C) & voltage (V) are interchanged & its reading is noted as negative.

- The induction motor is indirectly loaded by loading the d.c. generator, i.e., close the load switch  $S_2$  & with the help of loading rheostat, the d.c. generator is loaded in steps until the ammeters  $I_1$  and  $I_2$  read the rated current of the induction motor. At each step, the d.c. generator terminal voltage is maintained constant at its rated value (220V) using  $R_g$  and the readings of all the meters and speed are noted.
- The load is decreased in steps, maintaining the terminal voltage of the d.c. generator constant using  $R_g$  and the load switch  $S_2$  is opened.
- Now,  $R_g$  is brought to cut in position then, induction motor is stopped using the starter & the supply switch  $S_1$  is opened.
- The d.c. generator armature resistance ( $R_a$ ) is measured across A-A using multimeter.

**Tabular Column:**

Sl. No	$V_{t1}$ Volts	$I_1$ Amps	$I_2$ Amps	$W_1 = W_{R1} \times K_1$ Watts	$W_2 = W_{R2} \times K_2$ Watts	$V_L$ Volts	$I_L$ Amps	$I_2$ Amps	N rpm	$\% \eta$	BHP (HP)	T N-m	% slip	P.F.
1														
2														
3														
4														
5														

$R_a = \text{_____ } \Omega$ ,  $W_{R1}$  &  $W_{R2}$  - Wattmeter Readings.

$K_1$  &  $K_2$  = Wattmeter constants =  $\left[ \frac{(\text{Voltage range}) \times (\text{Current range}) \times (\text{p.f. of wattmeter})}{\text{Full scale divisions of wattmeter}} \right]$

**Calculations:**

From No-Load Readings:

$P_{NL}$  = No load losses of the d.c. generator =  $\frac{W_1 + W_2}{2} = \text{_____ Watts}$

From Load Readings:

$P_{ca}$  = Armature copper loss of d.c. generator =  $(I_a + I_g)^2 \times R_a = \text{_____ Watts}$

$P_{cg}$  = Power output of the d.c. generator =  $V_t \times I_L = \text{_____ Watts}$

$P_{om}$  = Power output of induction motor = Power input to d.c generator =  $P_{cg} + P_{ca} + P_{NL} = \text{_____ Watts}$

$P_{in}$  = Power input to the induction motor =  $W_1 + W_2 = \text{_____ Watts}$

Percentage efficiency of the induction motor =  $\% \eta = \frac{P_{out}}{P_{in}} \times 100 = \text{_____ } \%$

B.H.P =  $\frac{P_{out}}{735.5} = \text{_____ H.P.}$

Torque (T) =  $\frac{P_{out} \times 60}{2\pi \times N} = \text{_____ N-m}$

$$N_s = \text{Synchronous speed of induction motor} = \frac{120 \times f}{p} = \text{--- rpm}$$

$$\% s = \text{Percentage slip of induction motor} = \frac{N_s - N}{N_s} \times 100 = \text{--- \%}$$

$$\varphi = \text{Power factor (p.f.) angle} = \tan^{-1} \left[ \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} \right] \text{ in deg}$$

$$\text{p.f.} = \text{Power factor} = \cos \varphi$$

**Graphs:**

